 


Lab. Script 9

VHDL

COMBINATORIAL CIRCUITS


Observe the following combinatorial circuit composed only by elemental logic gates:



- Implement the circuit in VHDL.
- Establish a “testbench” to the circuit and simulate its response forcing all the possible combinations to its input.
- Establish an alternative architecture to the circuit that emulates only its behaviour (suggestion: use the reserved word WHEN)

SEQUENTIAL CIRCUITS

 Using VHDL draw an architecture that describes the behaviour of a D flip-flop active to the ascending edge.



Write a “testbench” to the previous circuit and simulate its operation.

RESOLUTION

```
-- CIRCUIT -----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity circuitoxor is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          Y : out STD_LOGIC);
end circuitoxor;

architecture Behavioral of circuitoxor is

begin

Y<=(A and not B) or (not A and B);

end Behavioral;

-- TESTBENCH -----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY testbench IS
END testbench;

ARCHITECTURE behavior OF testbench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT circuitoxor
    PORT(
        A : IN  std_logic;
        B : IN  std_logic;
        Y : OUT std_logic
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic := '0';
    signal B : std_logic := '0';

    --Outputs
    signal Y : std_logic;

BEGIN



    -- Instantiate the Unit Under Test (UUT)
    uut: circuitoxor PORT MAP (
        A => A,
        B => B,
        Y => Y
```

);

A<='0', '1' after 20 ns, '0' after 40 ns;

B<='0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns;

END;

  

-- CIRCUIT - Behaviour -----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity circuitoXor is
    Port ( entrada : in  STD_LOGIC_VECTOR (1 downto 0);
          Y : out  STD_LOGIC);
end circuitoXor;

architecture Behavioral of circuitoXor is

begin

Y<= '0' WHEN entrada="00" ELSE
    '1' WHEN entrada="01" ELSE
    '1' WHEN entrada="10" ELSE
    '0';
end Behavioral;
```

-- TESTBENCH -----

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY testbench IS
END testbench;

ARCHITECTURE behavior OF testbench IS
```

```

COMPONENT circuitoXor
PORT(
    entrada : IN  std_logic_vector(1 downto 0);
    Y : OUT  std_logic
);
END COMPONENT;

--Inputs
signal entrada : std_logic_vector(1 downto 0) := (others => '0');


--Outputs
signal Y : std_logic;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: circuitoXor PORT MAP (
        entrada => entrada,
        Y => Y
    );

    entrada<="00","01" after 10 ns,"10" after 20 ns,"11" after 30
ns,"00" after 40 ns;

END;
```

 

```

-- FLIP-FLOP D -----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity flipflopD is
    Port ( D : in  STD_LOGIC;
          CLK : in  STD_LOGIC;
          Q : out STD_LOGIC;
          nQ : out STD_LOGIC);
end flipflopD;

architecture Behavioral of flipflopD is

begin

process (CLK)

begin
    if (CLK'EVENT AND CLK='1') THEN
        Q<=D;
        nQ<=not D;
    end if;

end process;
```

```

end process;

end Behavioral;

-- TESTBENCH -----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY tb IS
END tb;

ARCHITECTURE behavior OF tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT flipflopD
    PORT(
        D : IN  std_logic;
        CLK : IN  std_logic;
        Q : OUT  std_logic;
        nQ : OUT  std_logic
    );
    END COMPONENT;

    --Inputs
    signal D : std_logic := '0';
    signal CLK : std_logic := '0';

    --Outputs
    signal Q : std_logic;
    signal nQ : std_logic;

```

BEGIN

